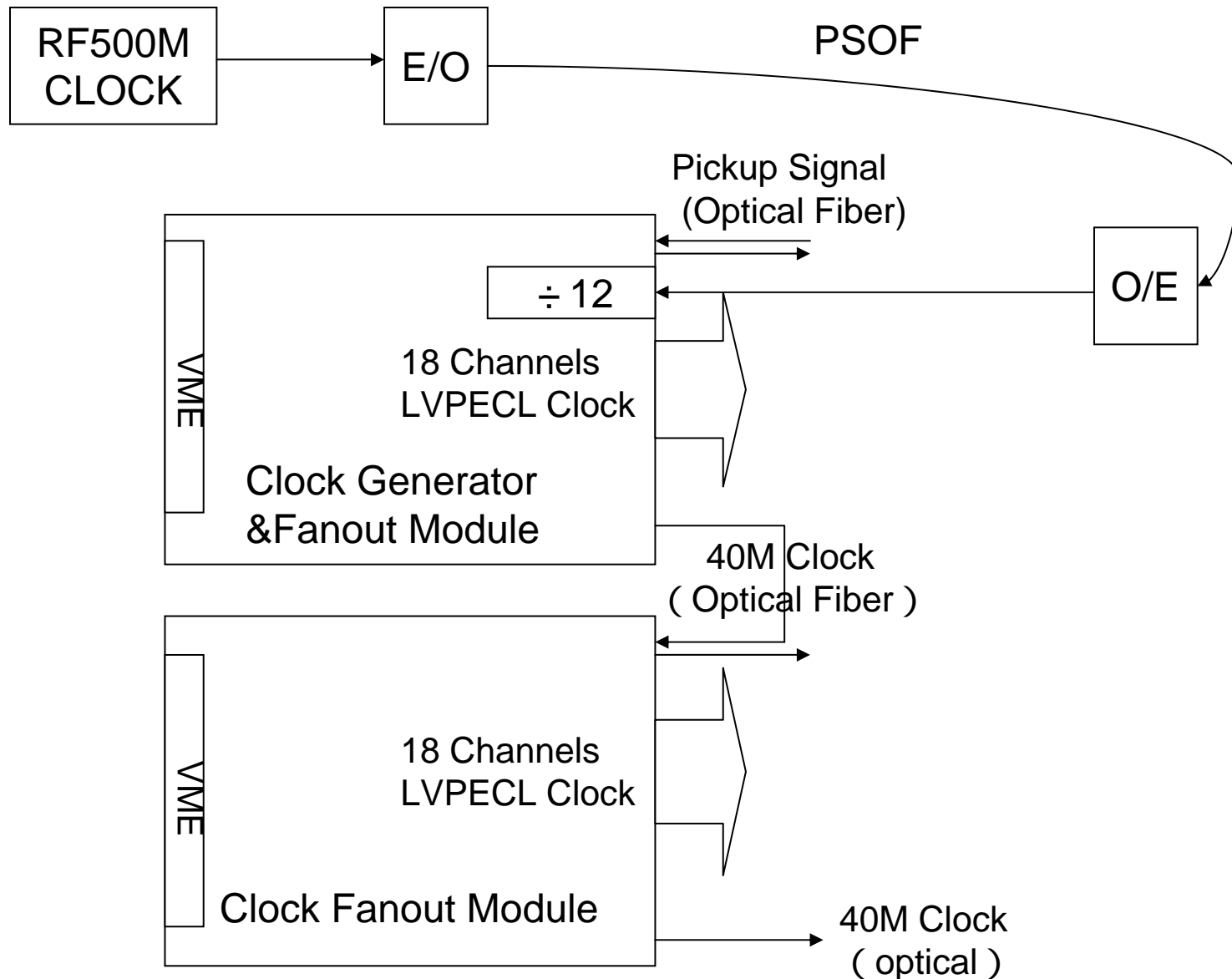


# Improved Design For BESIII Clock Generator Module

Li Hao

2006.04.27

# Diagram of BESIII Clock System



# Function of the Clock G&F Module


## Master module (clock generator & fanout module)

1. Receive system clock (499.8MHz RF signal) and Pickup signal.
2. Generate 41.65MHz clock from RF clock , synchronized with the rising edge of Pickup signal.
3. 1:20 Fanout (18 Diff LVPECL and 2 Optical outputs)


## Slave module (clock fanout module)

1. Receive 41.65MHz clock from clock G&F module.
2. 1:20 Fanout (18 Diff LVPECL and 2 Optical outputs)

# Scheme of Clock G&F Module

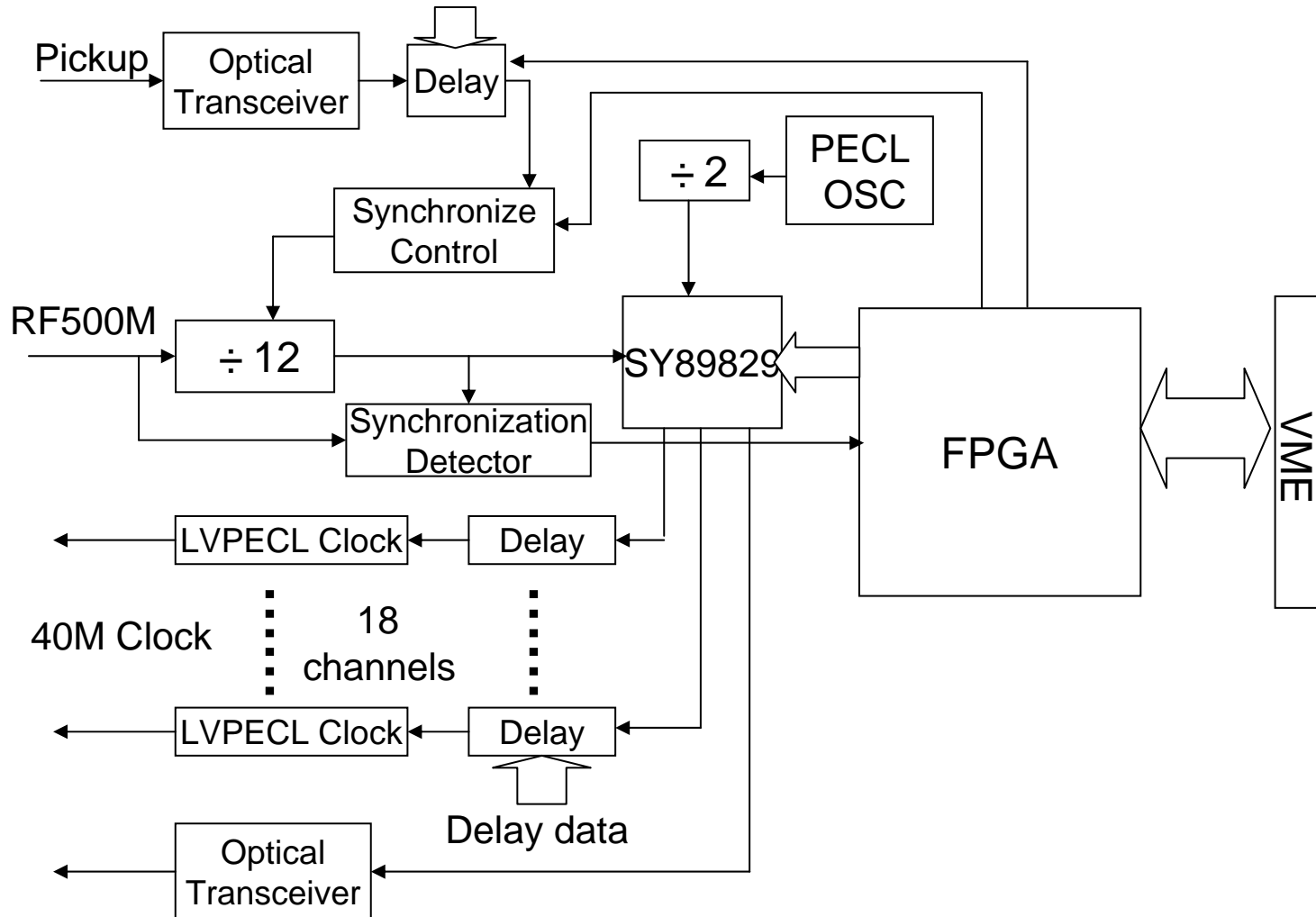


# Scheme of Clock Fanout Module

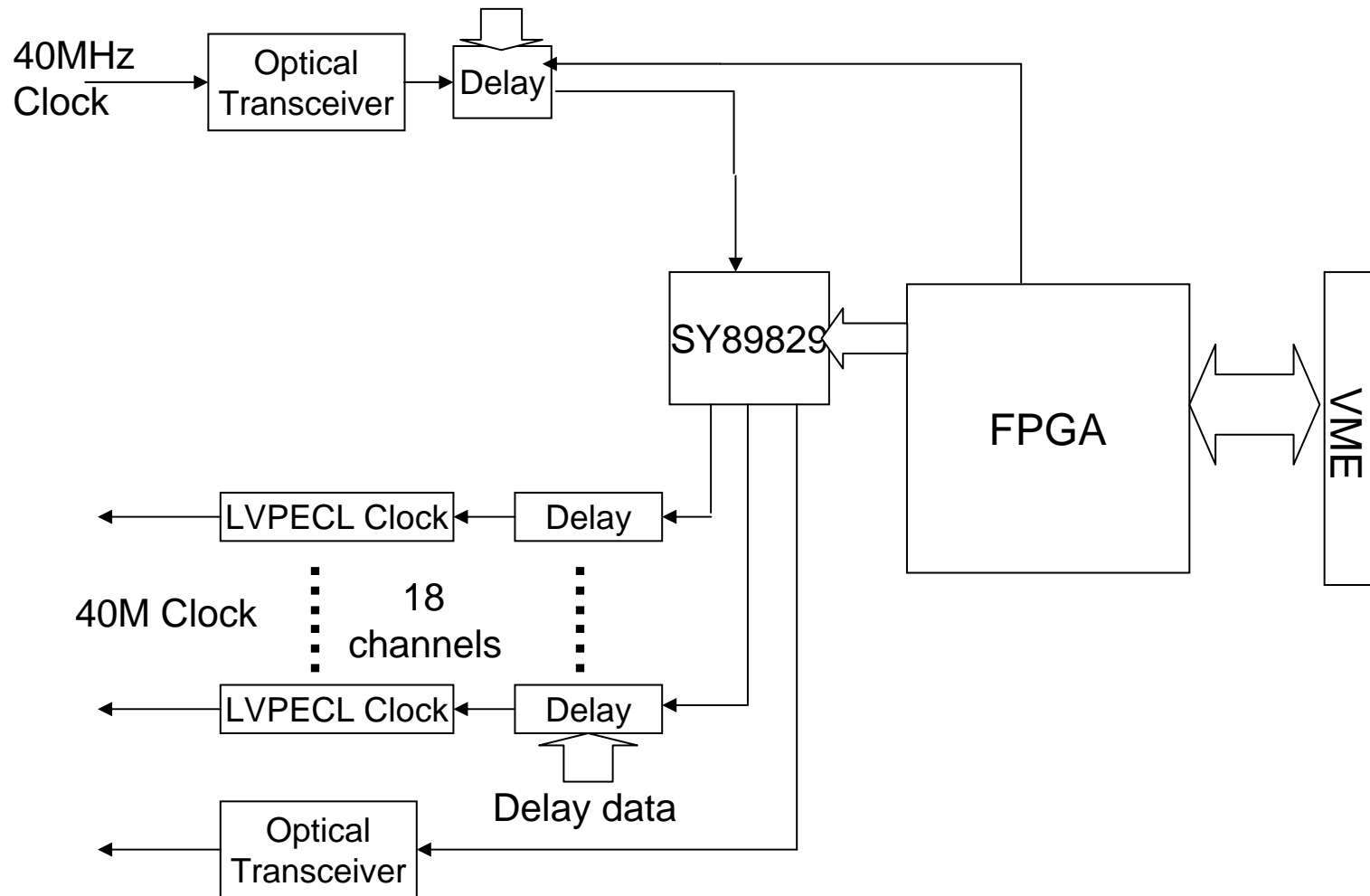

# Improvement on new G&F Module

1. According to the advice of international review, the clock divider's synchronization logic will be implemented with ECLinPS devices, rather than FPGA
2. A flag is appended for synchronization status indication.
3. According to VME64 XP specification, modify FPGA's logic.


# What does 'Synchronize' mean?

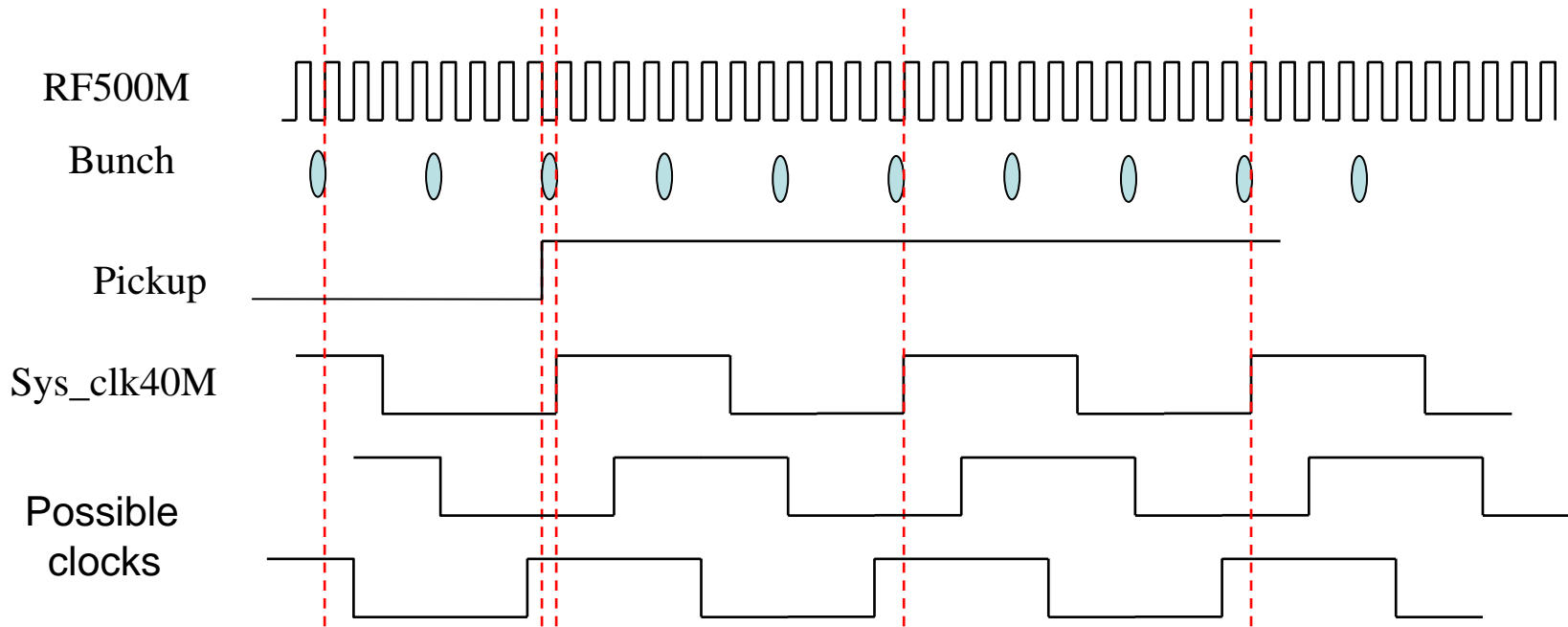

One bunch comes every 4 RF clock cycles.


There are 12 possible clocks if no Synchronization

# How to Synchronize & Detect It

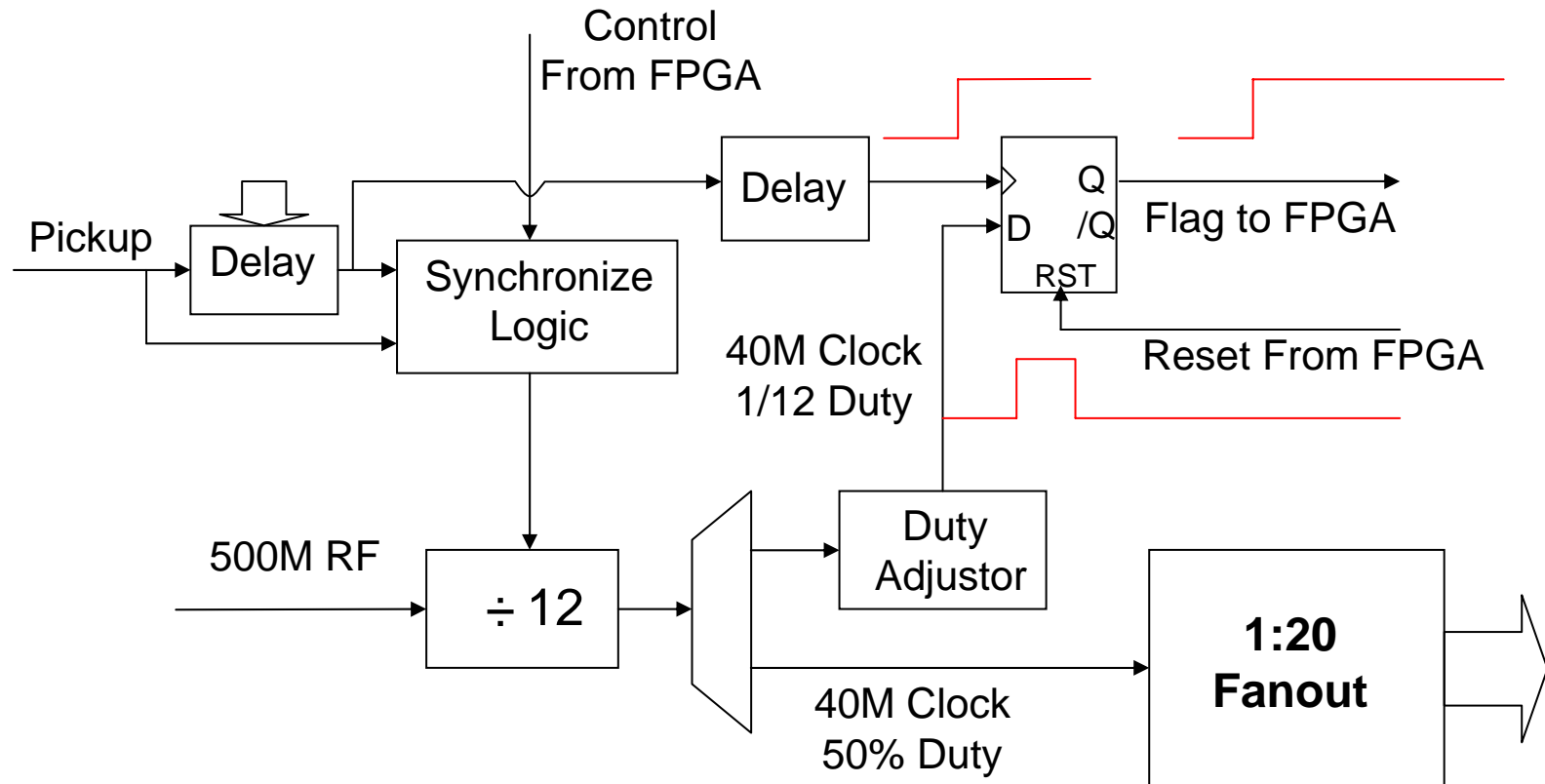




# Schematic of Synchronization Circuit

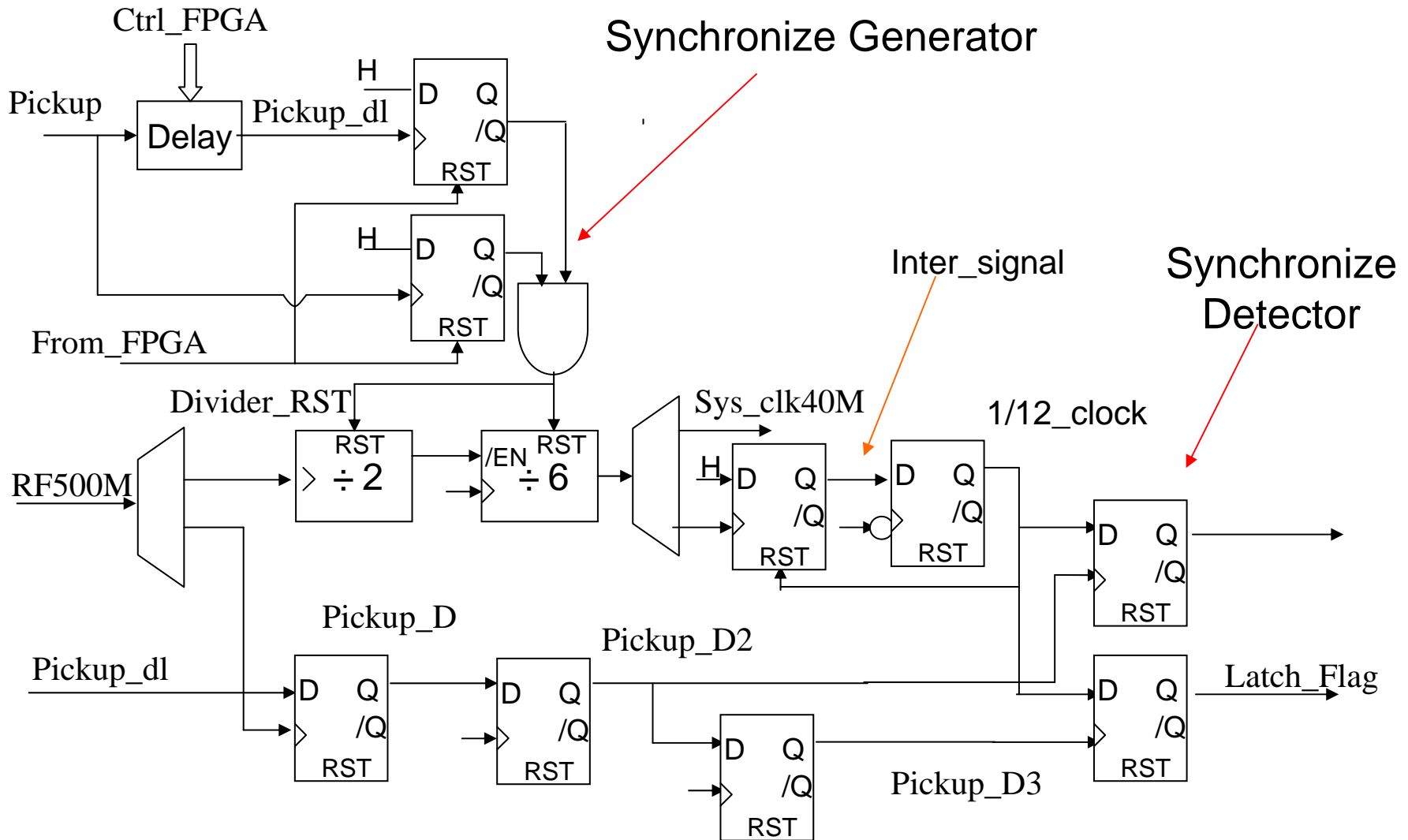

# Ideal Timing Diagram

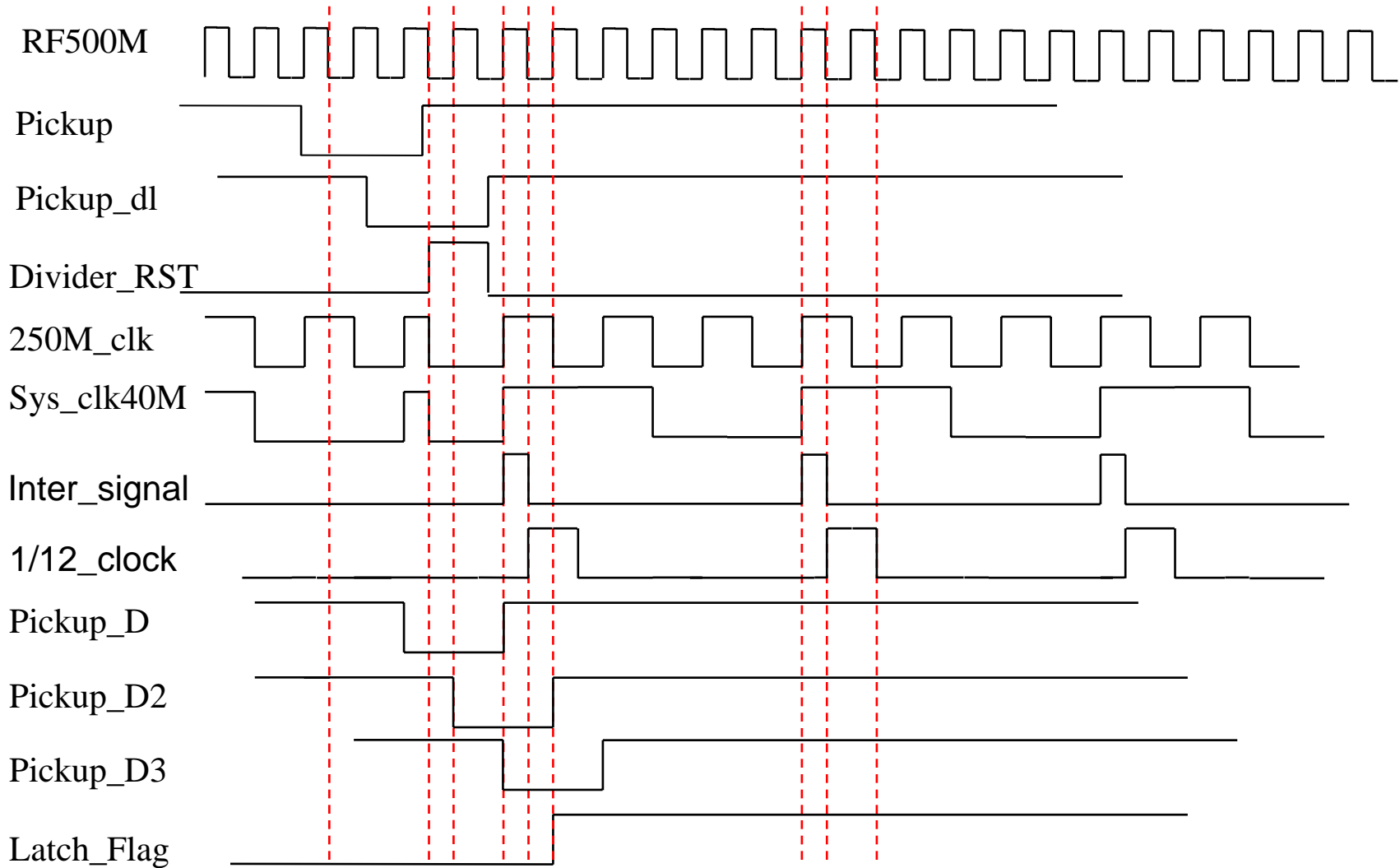

# Performance of ECLinPS Chips

## 1. MC100EP32 ECL $\div 2$ divider

CLK to Q /Q 350~450ps Reset to Q 400~480ps  $T_{RR}$  175ps

 


Figure 2. Timing Diagram

## 2. MC100EP139 ECL $\div 2/4$ , $\div 4/5/6$ clock generation chip

CLK to Q /Q 600~900ps Reset to Q 700~1000ps  $T_{RR}$  100~200ps

$t_{Set}$  /EN->/CLK 120~200ps  $t_{Hold}$  /CLK->/EN 50~100ps

## 3. MC100EP29 dual Differential clock and data Flip-Flop with set and reset


CLK to Q /Q 420~500ps  $t_{Set}$  / $t_{Hold}$  20~100ps

## 4. MC100EP131 Quad D Flip-Flop With Set, Reset, and Differential Clock

$C_{0-3}$  380~580ps;  $C_C$  400~600ps;  $R_{0-3}$  380~580ps; Set 380~580ps;

$t_{Set}$  / $t_{Hold}$  120~80ps

# Timing Diagram With Chip's Delay

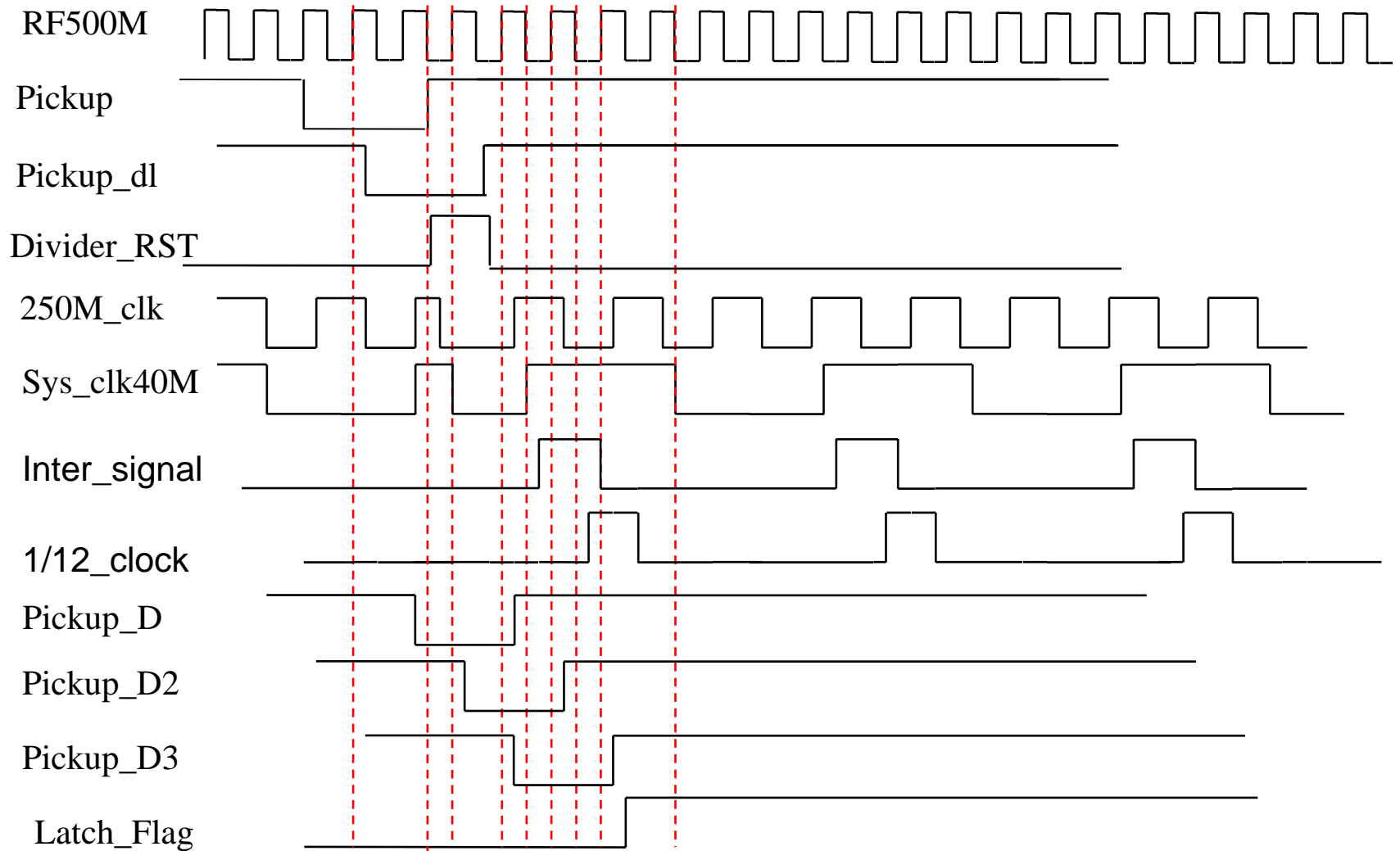

# Keystones about the design

## 1. Time margin

At least 500ps due to ECLinPS devices

$$T_{\text{wire}} = 2\text{ns} - 500\text{ps} - \text{Jitter}_{\text{pickup}}$$


if  $\text{Skew}_{\text{pickup}} > 500\text{ps}$ , then  $T_{\text{wire}} < 1\text{ns}$  !!!

## 2. PCB layout

wire delay

signal integrity

# PCB Layout of Clock Generator Module

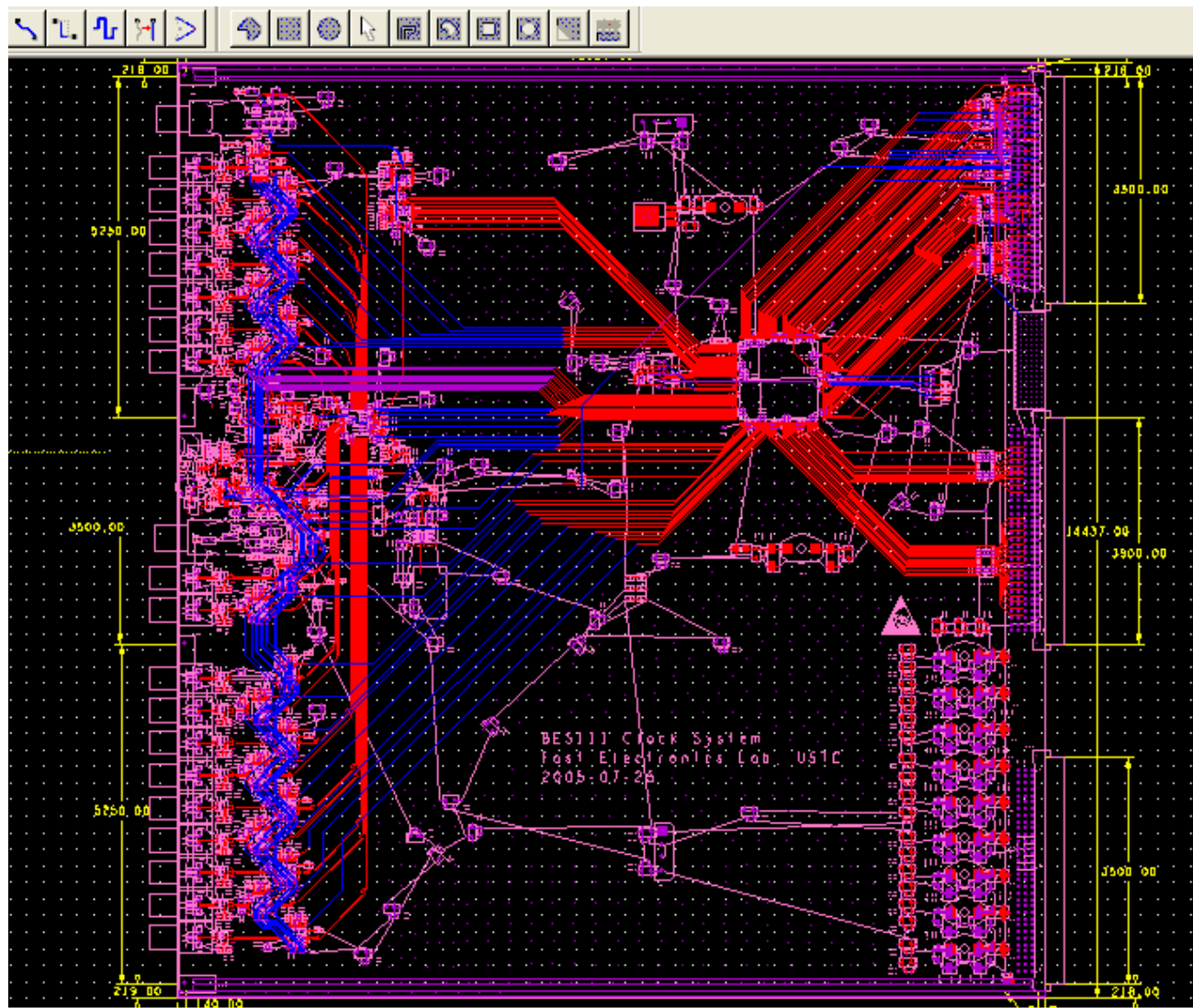

drawn 4.00, 4.00 apart for enhanced viewability.

# Schedule of this task

Schematic design (completed)

PCB Layout (will be completed before 5.10)

Debugging the modules (before 6.10)

Backup module Fabrication (after 6.10)

Thank you